

Full Adder Truth					lable	
	а	Ь	C	sum	carr	
	0	0	0	0	0	
	0	0	1	1	0	
	0	1	0	1	0	
	0	1	1	0	1	
	1	0	0	1	0	
	1	0	1	0	1	
	1	1	0	0	1	
	1	1	1	1	1	

